



UNIVERSITY COLLEGE LONDON

MENG MECHANICAL ENGINEERING

MECH0071 ELECTRICAL POWER SYSTEMS AND ELECTRICAL PROPULSION

## PSCAD COURSEWORK

*Author:*  
Hasha Dar

*Module coordinator:*  
Prof. Richard Bucknall

November 28, 2022

## Contents

<b>List of Figures</b>	<b>2</b>
<b>List of Tables</b>	<b>2</b>
<b>1 Diode bridge circuit</b>	<b>3</b>
1.1 Circuit diagram . . . . .	3
1.2 Instantaneous voltages . . . . .	3
1.3 Effect of increasing capacitance to 25 $\mu\text{F}$ . . . . .	4
<b>2 Equivalent transformer</b>	<b>5</b>
2.1 Circuit diagram . . . . .	5
2.2 Resistive load . . . . .	5
2.2.1 RMS Voltage . . . . .	5
2.2.2 Power factor . . . . .	6
2.3 Inductive load . . . . .	6
2.3.1 RMS Voltage across the load . . . . .	6
2.3.2 Power factor across the load . . . . .	7
2.4 Capacitive load . . . . .	8
2.4.1 RMS Voltage . . . . .	8
2.4.2 Power factor . . . . .	8
<b>A MATLAB code</b>	<b>10</b>
A.1 Question 1 . . . . .	10
A.2 Question 2 . . . . .	10

## List of Figures

1	Circuit diagram to show diode bridge circuit. . . . .	3
2	Graph to show instantaneous input voltage across the voltage source. . . . .	3
3	Graph to show instantaneous output voltage across the resistive load. . . . .	4
4	Graph to show comparison between instantaneous output voltage across the resistive load for different capacitance values. . . . .	4
5	Circuit diagram to show equivalent transformer. . . . .	5
6	Voltage across load over time and value of $V_{RMS,r}$ . . . . .	5
7	Power factor over time (resistor). . . . .	6
8	Voltage across load over time and value of $V_{RMS,i}$ . . . . .	7
9	Power factor over time (inductor). . . . .	7
10	Voltage across load over time and value of $V_{RMS,c}$ . . . . .	8
11	Power factor over time (capacitor). . . . .	9

## List of Tables

# 1 Diode bridge circuit

## 1.1 Circuit diagram

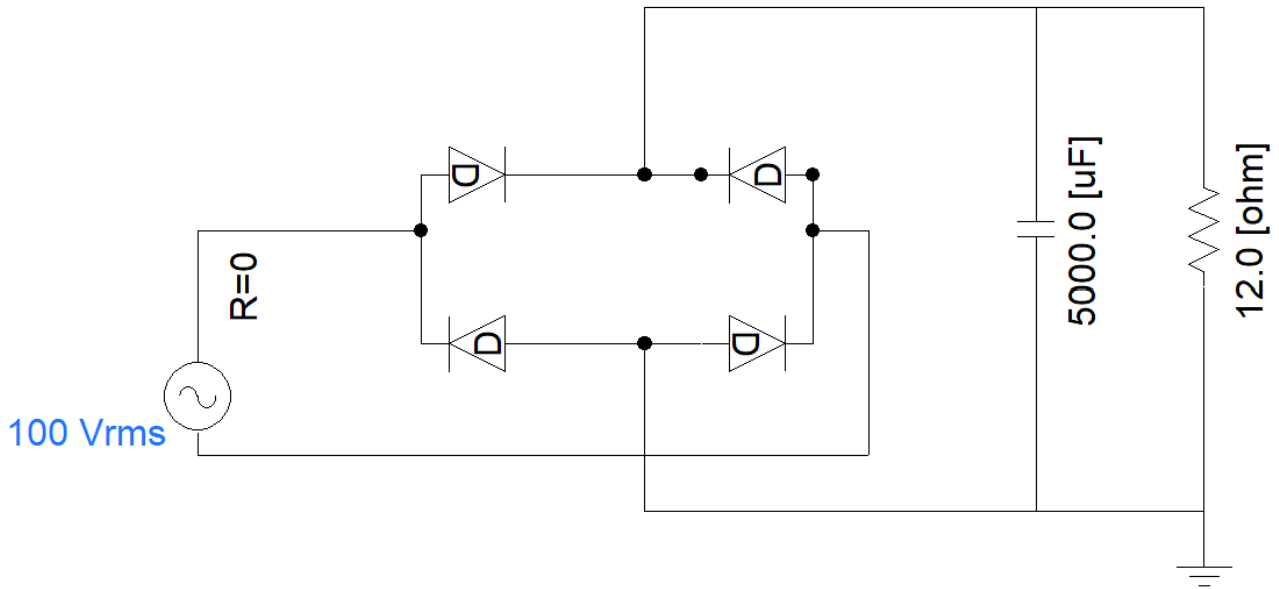


Figure 1: Circuit diagram to show diode bridge circuit.

## 1.2 Instantaneous voltages

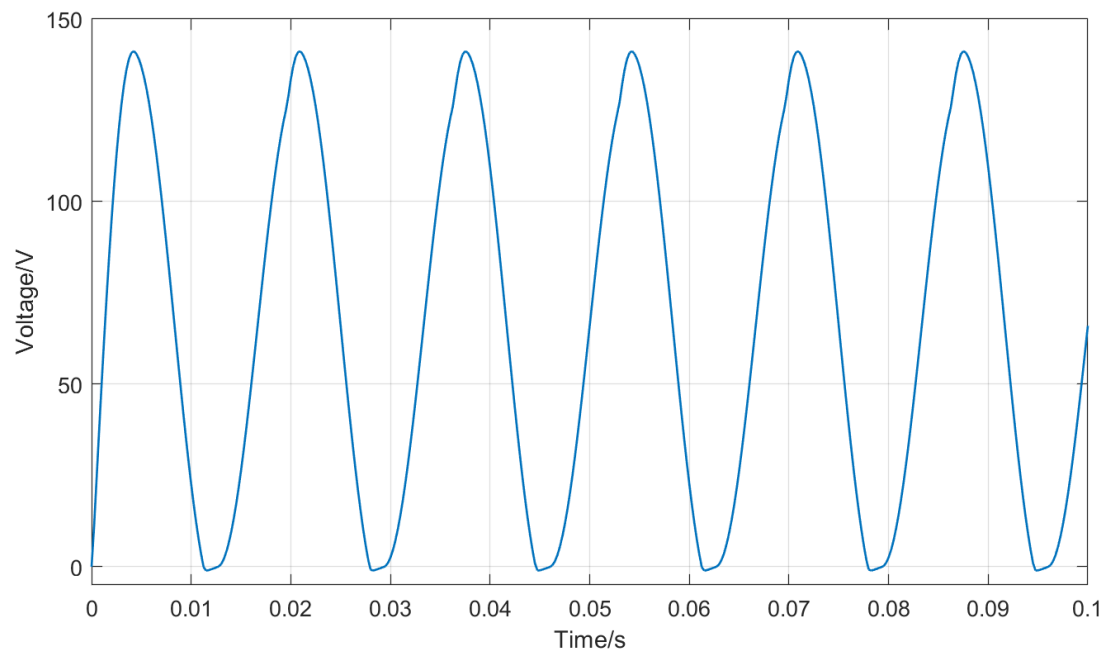


Figure 2: Graph to show instantaneous input voltage across the voltage source.

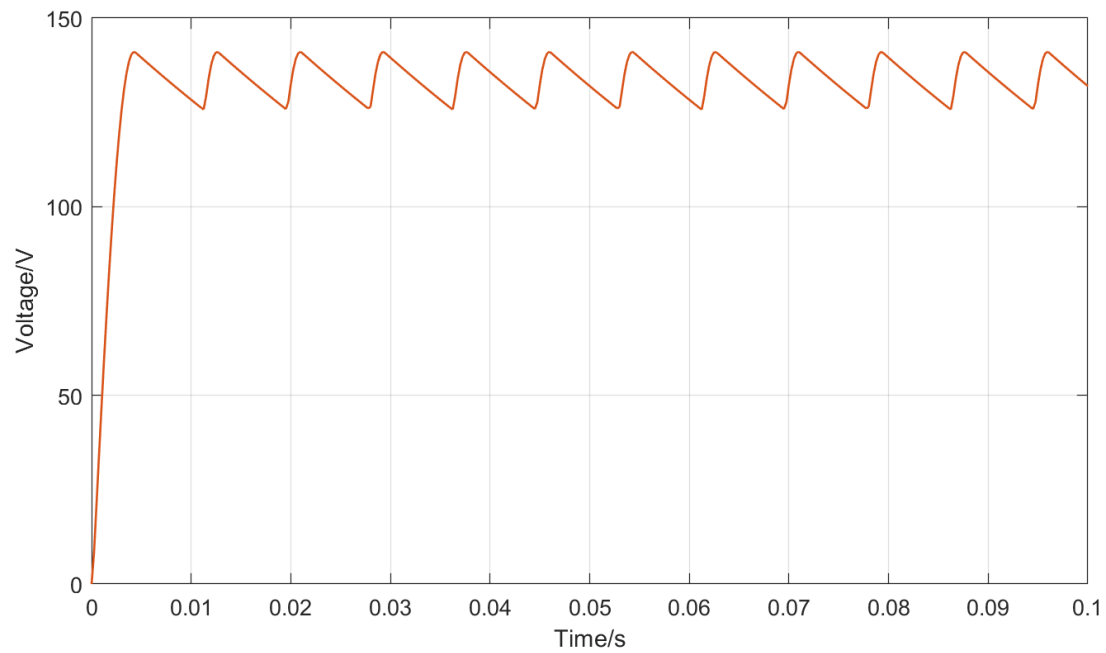


Figure 3: Graph to show instantaneous output voltage across the resistive load.

### 1.3 Effect of increasing capacitance to 25 $\mu\text{F}$

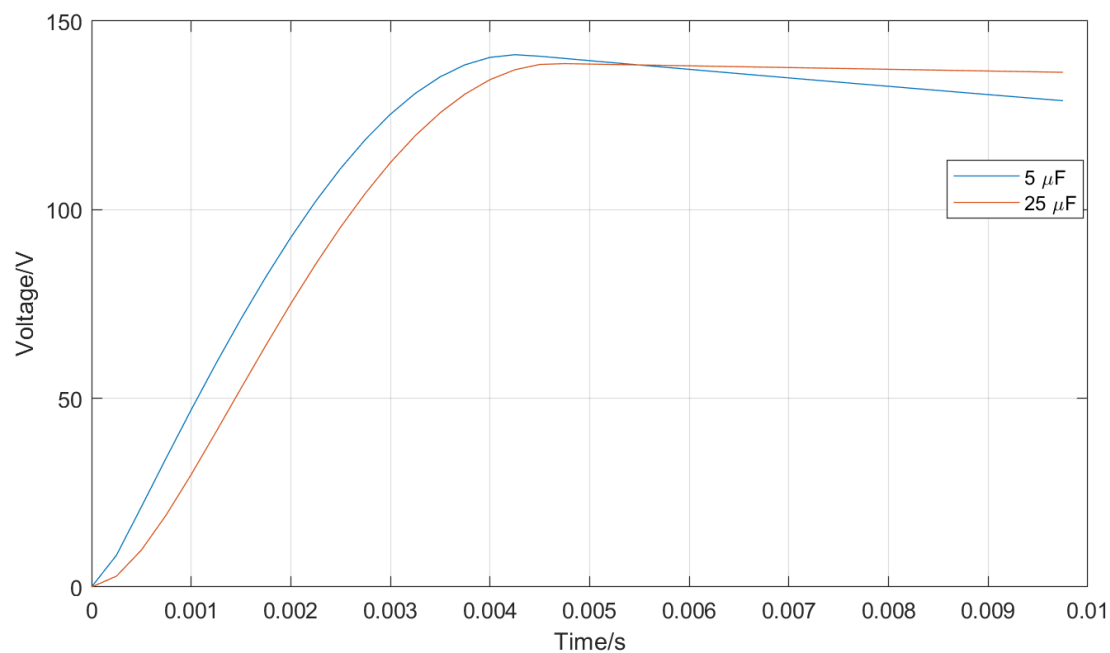


Figure 4: Graph to show comparison between instantaneous output voltage across the resistive load for different capacitance values.

The purpose of the capacitor in this diode bridge circuit is to filter/reduce the amount of voltage ripple, inherent to bridge diode circuits. We can see in Figure 3 that our voltage drop is approximately 25 V between pulses (5  $\mu\text{F}$ ). By increasing the capacitance, our voltage drop reduces (from data: voltage drop with 25  $\mu\text{F}$   $\approx$  4 V.) This is desirable as this achieves a more stable DC output. However, increasing the capacitance also increases the rise time and reduces the peak voltage of the output, shown in Figure 4.

## 2 Equivalent transformer

### 2.1 Circuit diagram

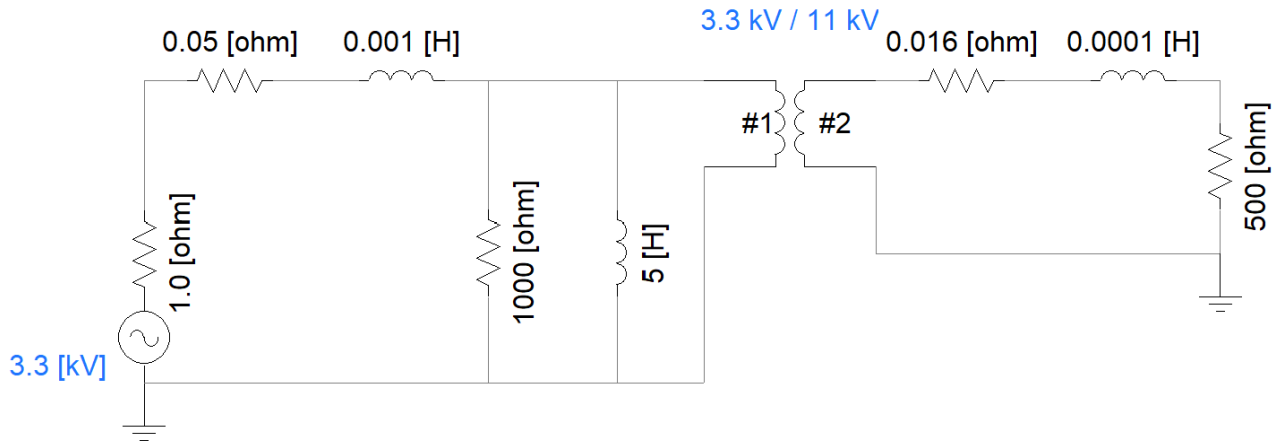


Figure 5: Circuit diagram to show equivalent transformer.

### 2.2 Resistive load

#### 2.2.1 RMS Voltage

The RMS voltage can be calculated using (1).

$$V_{RMS} = \sqrt{\frac{\sum_{i=1}^n x_i^2}{n}} \quad (1)$$

- Simulation time: 0.5 s
- Number of data points ( $n$ ): 2002

Using MATLAB:

$$V_{RMS,r} = 10.14 \text{ kV} \quad (2)$$

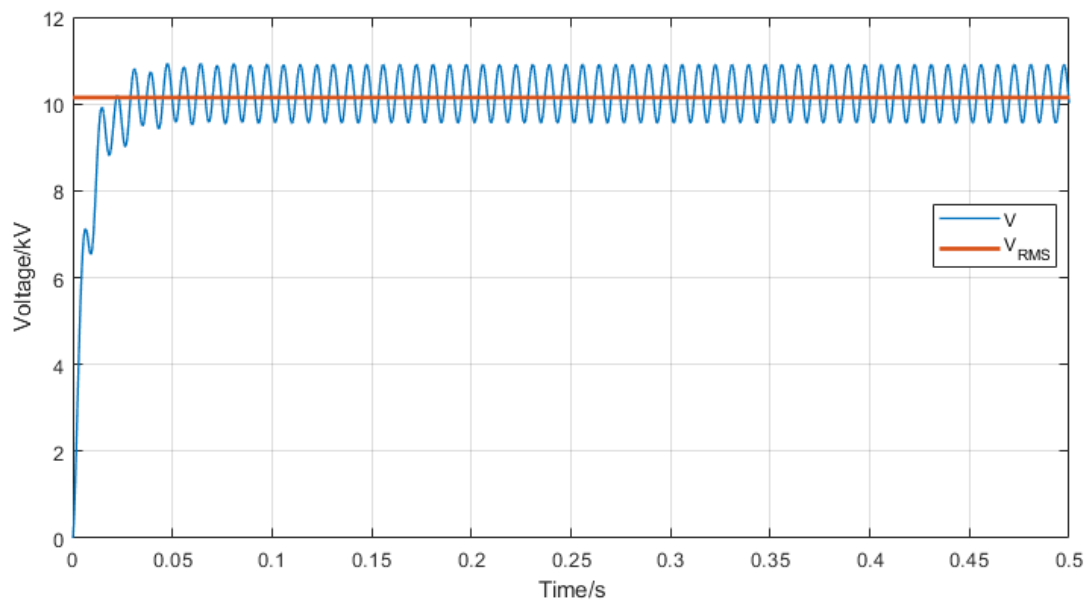


Figure 6: Voltage across load over time and value of  $V_{RMS,r}$ .

(see Appendix A.2)

### 2.2.2 Power factor

The power factor can be calculated using the following equation:

$$PF = \cos \phi \quad (3)$$

Using MATLAB, the converged value of the power factor was found by averaging the final values in the dataset.

$$PF_r = 0.995 \quad (4)$$

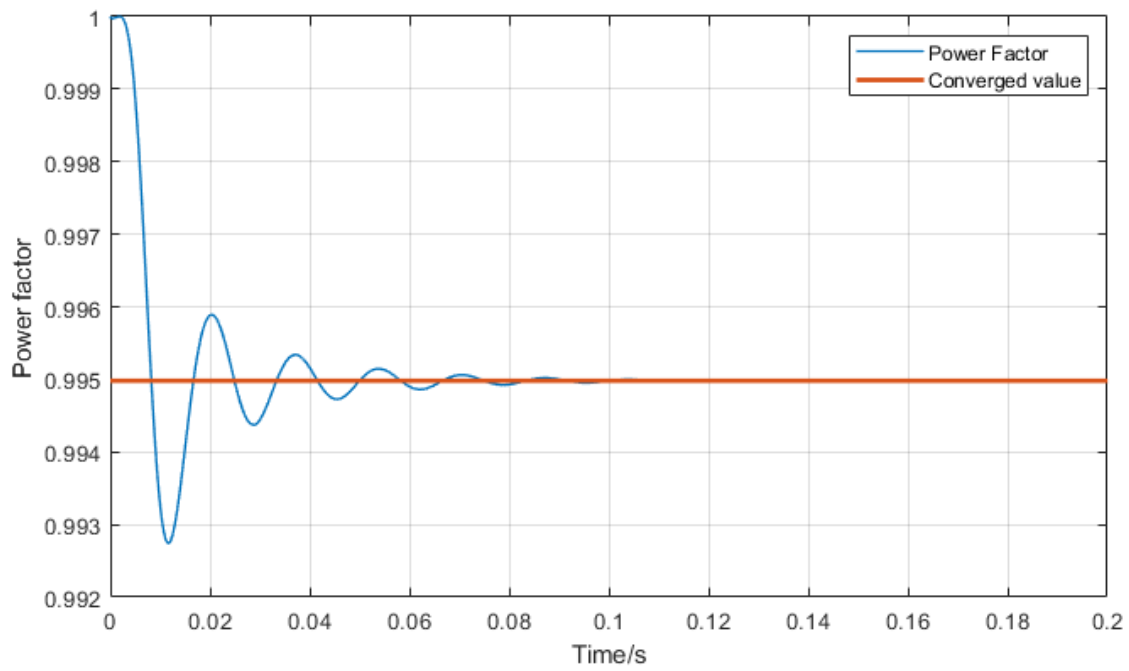


Figure 7: Power factor over time (resistor).

(see Appendix A.2).

## 2.3 Inductive load

### 2.3.1 RMS Voltage across the load

Using MATLAB:

$$V_{RMS,i} = 2.79 \text{ kV} \quad (5)$$

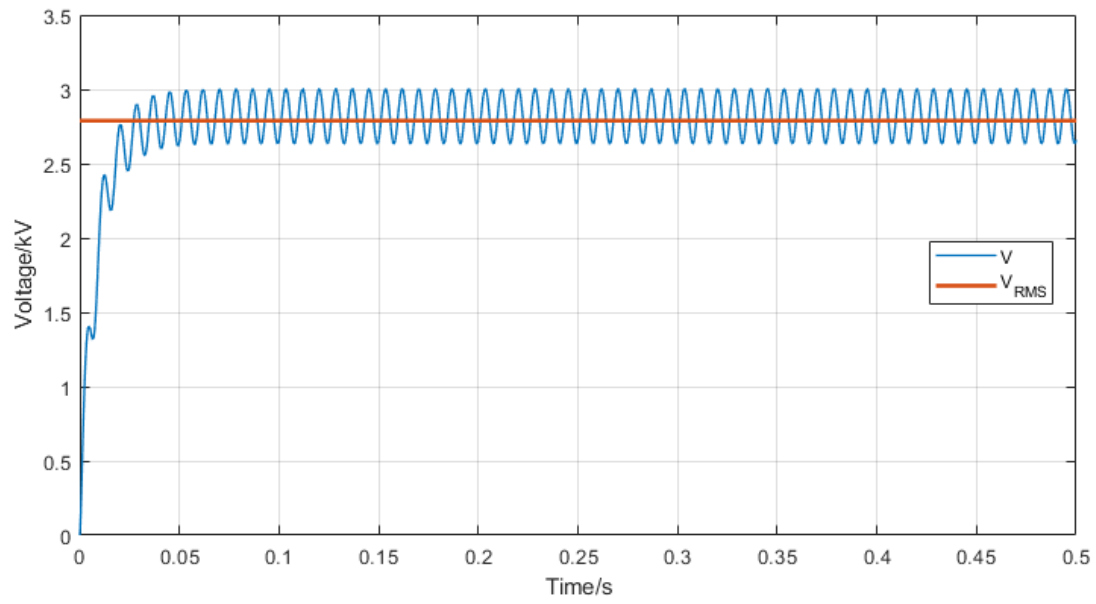


Figure 8: Voltage across load over time and value of  $V_{RMS,i}$ .

(see Appendix A.2)

### 2.3.2 Power factor across the load

Using MATLAB:

$$PF_i = 0.563 \quad (6)$$

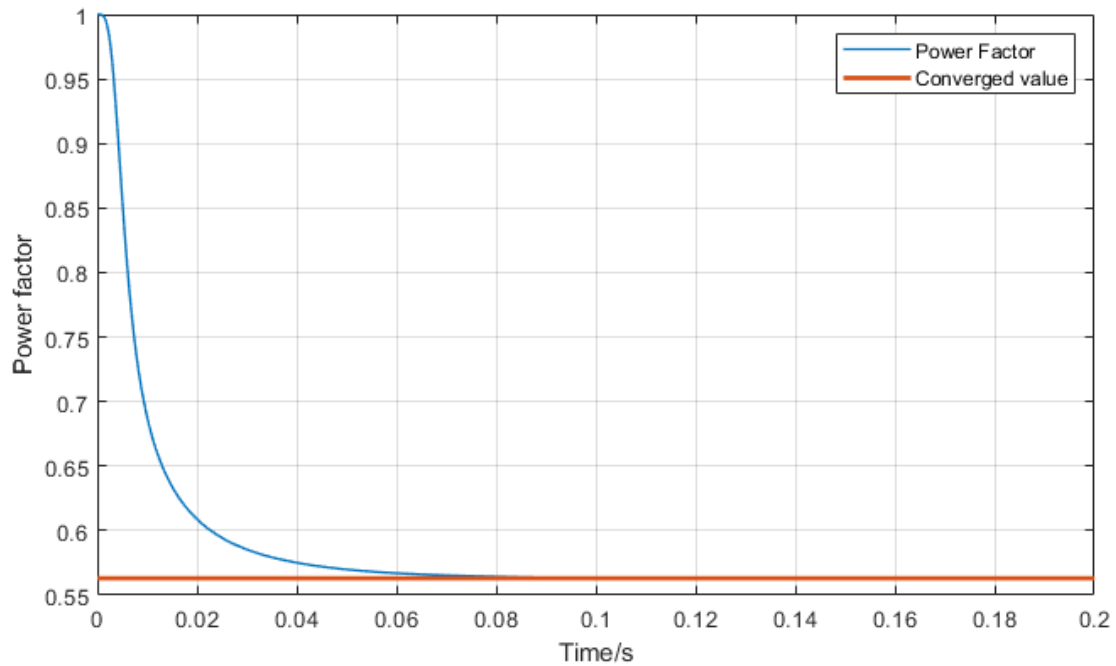


Figure 9: Power factor over time (inductor).

(see Appendix A.2).



## 2.4 Capacitive load

### 2.4.1 RMS Voltage

Using MATLAB:

$$V_{RMS,c} = 0.262 \text{ kV} \quad (7)$$

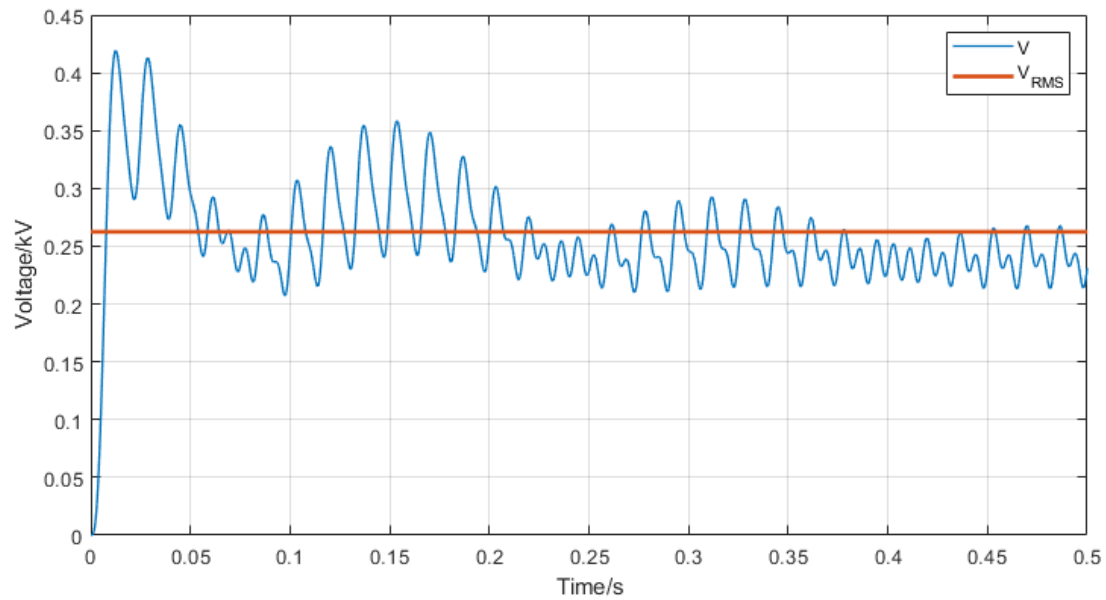


Figure 10: Voltage across load over time and value of  $V_{RMS,c}$ .

(see Appendix A.2)

### 2.4.2 Power factor

Using MATLAB:

$$PF_c = -0.328 \quad (8)$$

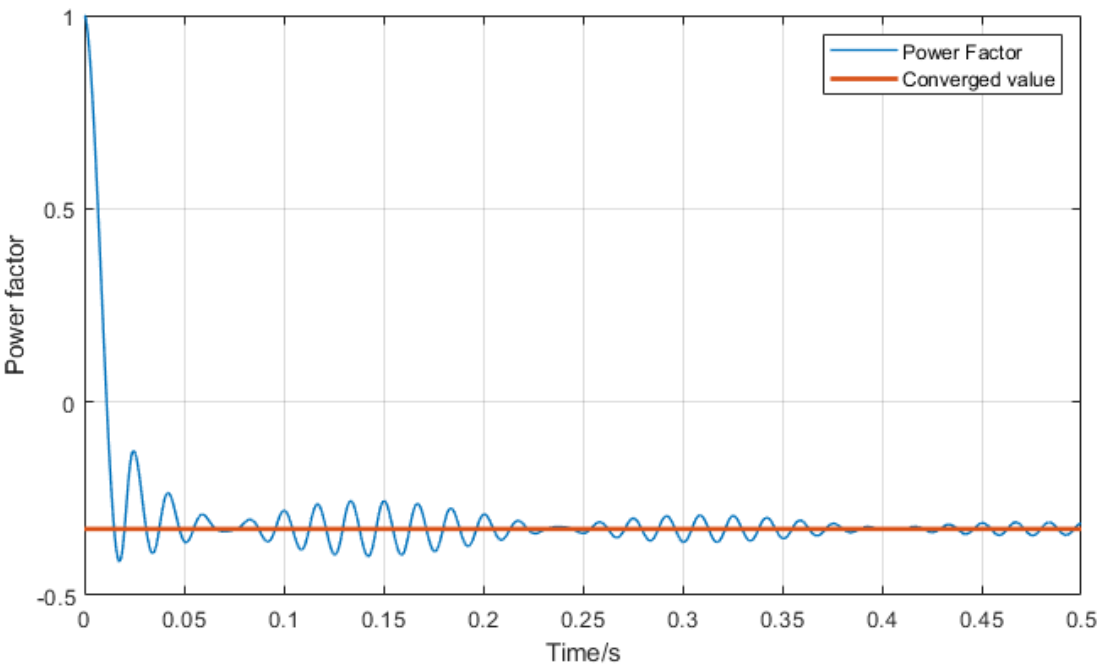


Figure 11: Power factor over time (capacitor).

(see Appendix A.2).

## A MATLAB code

### A.1 Question 1

---

```
%HD
clc
clear

%import data
data = readmatrix('dataimport.xlsx','Sheet','q1');

%datasets
VSource = cat(2,data(:,5),data(:,6));
VResistor = cat(2,data(:,7),data(:,8));
VResistor2 = cat(2,data(:,9),data(:,10));

%graph plots
%plot(VResistor2(:,1),VResistor2(:,2),'LineWidth',1,'color',[0.4940 0.1840
    0.5560])
plot(VResistor(1:40,1),VResistor(1:40,2),VResistor2(1:40,1),VResistor2(1:40,2))
grid on
axis 'auto xy'
xlim([0,0.01])
ylim([0,150])
xlabel('Time/s')
ylabel('Voltage/V')
legend('5 {\mu}F','25 {\mu}F')

%'color',[0.4940 0.1840 0.5560]
```

---

### A.2 Question 2

---

```
%HD
clc
clear

%import data
data = readmatrix('dataImport.xlsx','Sheet','table2');
data2 = readmatrix('dataImport.xlsx','Sheet','table2.2');

%datasets
VResistor = cat(2,data(:,1),data(:,2));
PhaseResistor = cat(2,data(:,3),data(:,4));
VInductor = cat(2,data2(:,1),data2(:,2));
PhaseInductor = cat(2,data2(:,3),data2(:,4));
VCapacitor = cat(2,data2(:,5),data2(:,6));
PhaseCapacitor = cat(2,data2(:,7),data2(:,8));

%VRMS
VSq1 = VResistor(:,2).^2;
VRMSResistor = sqrt(sum(VSq1)/numel(VSq1));

VSq2 = VInductor(:,2).^2;
VRMSInductor = sqrt(sum(VSq2)/numel(VSq2));

VSq3 = VCapacitor(:,2).^2;
VRMSCapacitor = sqrt(sum(VSq3)/numel(VSq3));

%PF
```

```
averagePFResistor =  
    cos(mean(PhaseResistor(0.8*numel(PhaseResistor(:,1)):end,2)));  
PFResistor = cos(PhaseResistor(:,2));  
  
averagePFInductor =  
    cos(mean(PhaseInductor(0.8*numel(PhaseInductor(:,1)):end,2)));  
PFInductor = cos(PhaseInductor(:,2));  
  
averagePFCapacitor =  
    cos(mean(PhaseCapacitor(0.8*numel(PhaseCapacitor(:,1)):end,2)));  
PFCapacitor = cos(PhaseCapacitor(:,2));  
  
%graph plotting  
%{  
plot(VCapacitor(:,1),VCapacitor(:,2),...  
    VCapacitor(:,1),linspace(VRMSCapacitor,VRMSCapacitor,numel(VCapacitor(:,1))))  
grid on  
axis 'auto xy'  
xlim([0,0.5])  
xlabel('Time/s')  
ylabel('Voltage/kV')  
legend('V','V_{RMS}')
```

---

```
%}  
  
plot(PhaseResistor(:,1),PFResistor,PhaseResistor(:,1),...  
    linspace(averagePFResistor,averagePFResistor,numel(PhaseResistor(:,1))))  
grid on  
axis 'auto xy'  
xlim([0,0.2])  
xlabel('Time/s')  
ylabel('Power factor')  
legend('Power Factor','Converged value')
```

---