



UNIVERSITY COLLEGE LONDON

MENG MECHANICAL ENGINEERING

MECH0071 ELECTRICAL POWER SYSTEMS AND ELECTRICAL PROPULSION

PSCAD COURSEWORK

Author:
Hasha Dar

Module coordinator:
Prof. Richard Bucknall

November 17, 2022

Contents

List of Figures	2
List of Tables	2
1 Diode bridge circuit	3
1.1 Circuit diagram	3
1.2 Instantaneous voltages	3
1.3 Effect of increasing capacitance to 25 μF	4
2 Equivalent transformer	5
2.1 Circuit diagram	5
2.2 RMS Voltage across the load	5
A MATLAB code	6
A.1 Question 1	6
A.2 Question 2	6

List of Figures

1	Circuit diagram to show diode bridge circuit.	3
2	Graph to show instantaneous input voltage across the voltage source.	3
3	Graph to show instantaneous output voltage across the resistive load.	4
4	Graph to show comparison between instantaneous output voltage across the resistive load for different capacitance values.	4
5	Circuit diagram to show equivalent transformer.	5

List of Tables

1 Diode bridge circuit

1.1 Circuit diagram

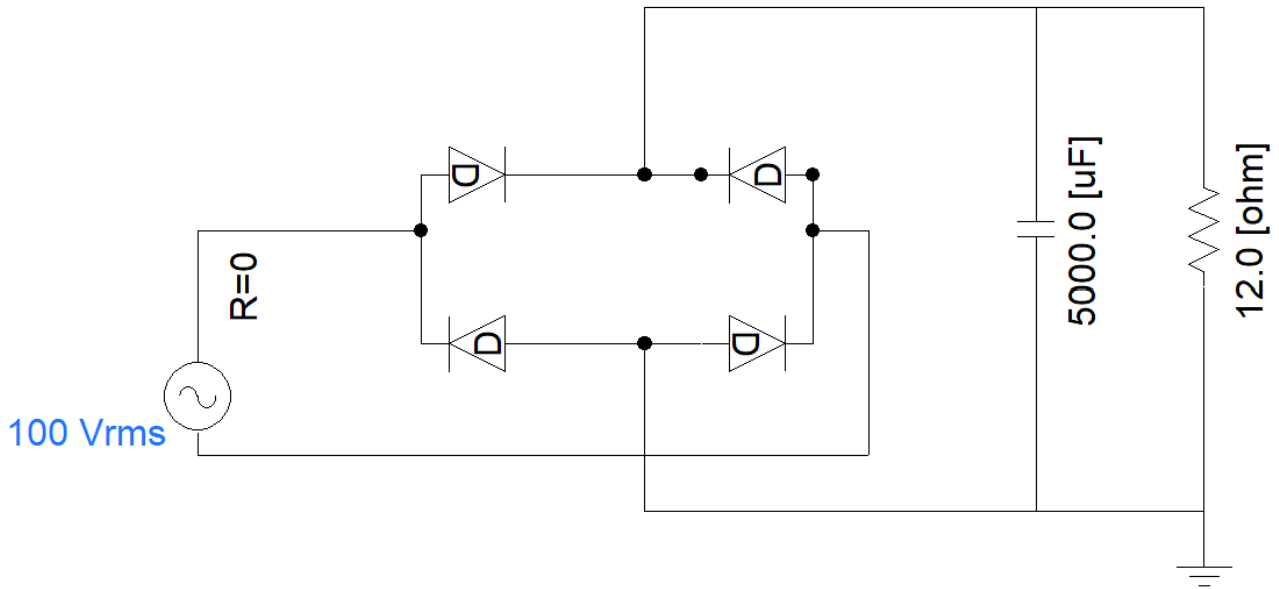


Figure 1: Circuit diagram to show diode bridge circuit.

1.2 Instantaneous voltages

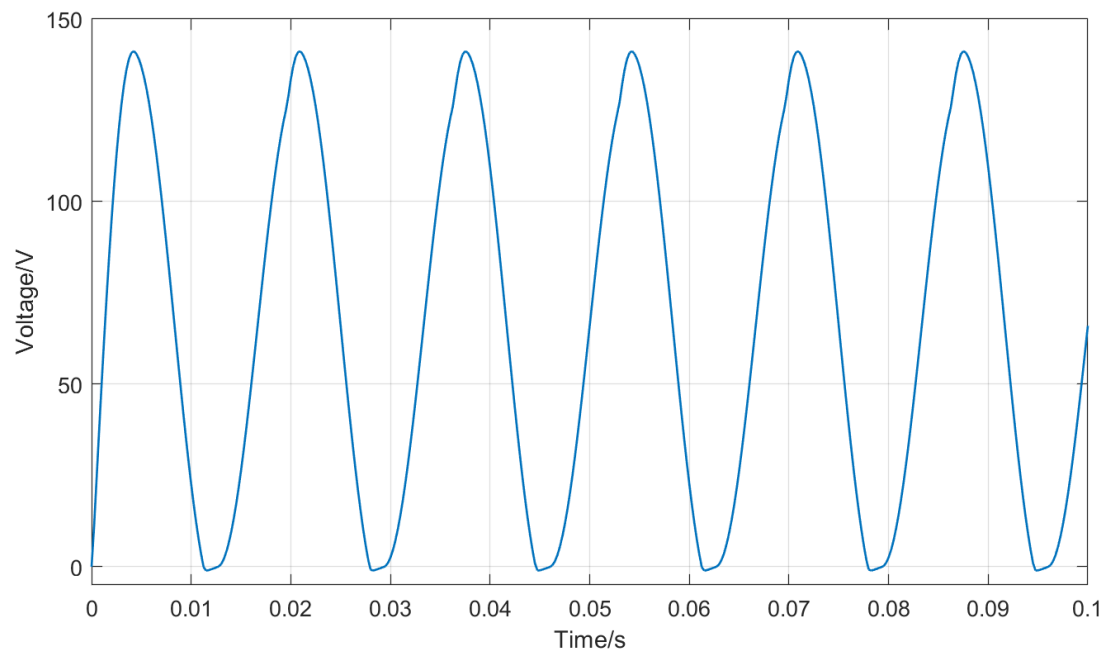


Figure 2: Graph to show instantaneous input voltage across the voltage source.

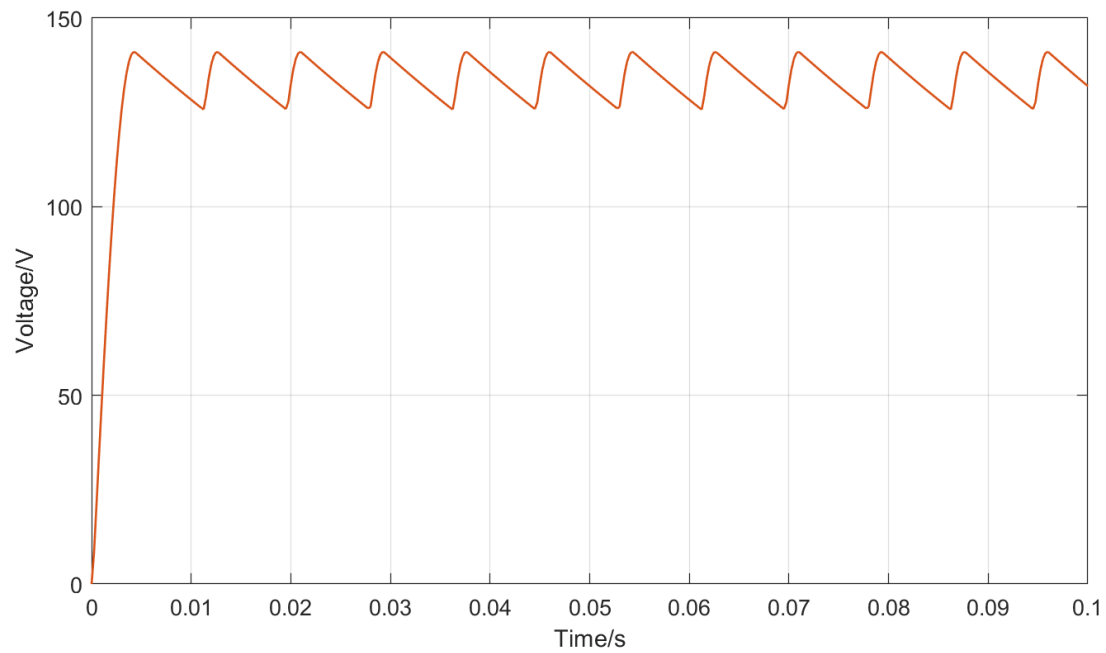


Figure 3: Graph to show instantaneous output voltage across the resistive load.

1.3 Effect of increasing capacitance to $25\text{ }\mu\text{F}$

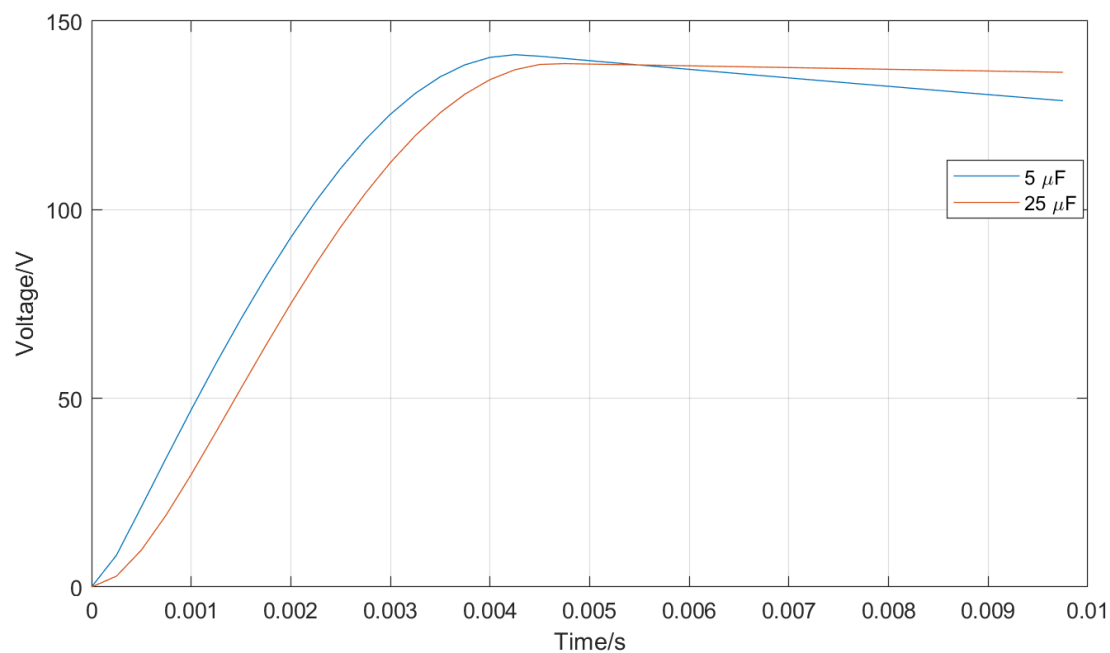


Figure 4: Graph to show comparison between instantaneous output voltage across the resistive load for different capacitance values.

The purpose of the capacitor in this diode bridge circuit is to filter/reduce the amount of voltage ripple, inherent to bridge diode circuits. We can see in Figure 3 that our voltage drop is approximately 25 V between pulses. By increasing the capacitance, our voltage drop reduces (from data: voltage drop with $25\text{ }\mu\text{F} \approx 4\text{ V}$.) This is desirable as this achieves a more stable DC output. However, increasing the capacitance also increases the rise time and reduces the peak voltage of the output, shown in Figure 4.

2 Equivalent transformer

2.1 Circuit diagram

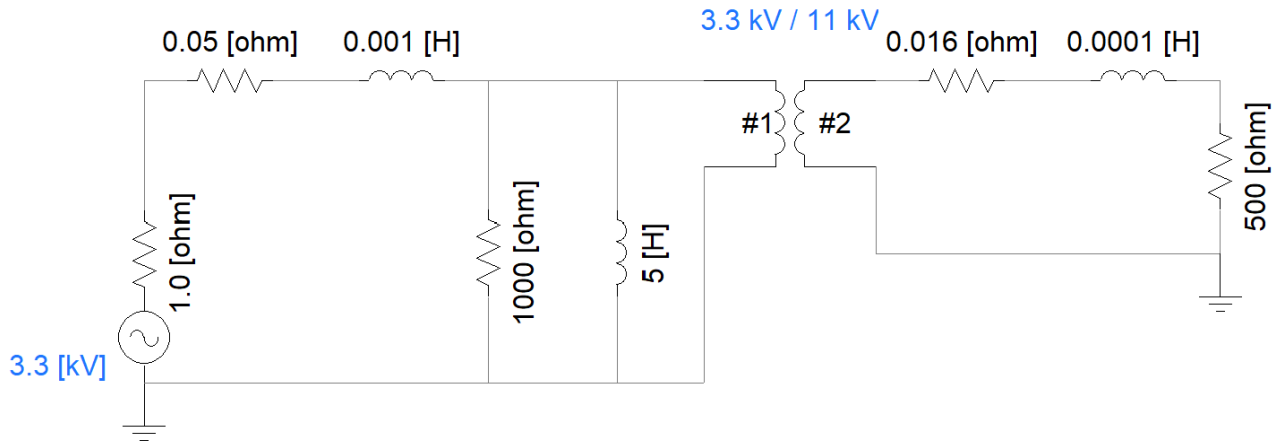


Figure 5: Circuit diagram to show equivalent transformer.

2.2 RMS Voltage across the load

Measuring the voltage across the load over 0.1 s, the voltage values were put into MATLAB (see Appendix A.2). The RMS voltage can be calculated using the following equation.

$$V_{RMS} = \sqrt{\frac{\sum_{i=1}^n x_i^2}{n}} \quad (1)$$

- Number of data points (n): 401
- Number of complete AC cycles in time frame: 6

$$V_{RMS,load} = 10.72 \text{ kV} \quad (2)$$

A MATLAB code

A.1 Question 1

```
%HD
clc
clear

%import data
data = readmatrix('dataimport.xlsx','Sheet','q1');

%datasets
VSource = cat(2,data(:,5),data(:,6));
VResistor = cat(2,data(:,7),data(:,8));
VResistor2 = cat(2,data(:,9),data(:,10));

%graph plots
%plot(VResistor2(:,1),VResistor2(:,2),'LineWidth',1,'color',[0.4940 0.1840
    0.5560])
plot(VResistor(1:40,1),VResistor(1:40,2),VResistor2(1:40,1),VResistor2(1:40,2))
grid on
axis 'auto xy'
xlim([0,0.01])
ylim([0,150])
xlabel('Time/s')
ylabel('Voltage/V')
legend('5 {\mu}F','25 {\mu}F')

%'color',[0.4940 0.1840 0.5560]
```

A.2 Question 2

```
%HD
clc
clear

%import data
data = readmatrix('dataImport.xlsx','Sheet','q2');

%datasets
VResistor = cat(2,data(:,5),data(:,6));
PhaseResistor = cat(2,data(:,7),data(:,8));

%VRMS
VSq1 = VResistor(:,2).^2;
VRMSResistor = sqrt(sum(VSq1)/numel(VSq1));

%PF
PFResistor = cos(PhaseResistor(:,2));

%graph plotting
plot(VResistor(:,1),VResistor(:,2))
grid on
axis 'auto xy'
xlim([0,0.1])
xlabel('Time/s')
ylabel('Voltage/kV')
```
