



UNIVERSITY COLLEGE LONDON

MENG MECHANICAL ENGINEERING

MECH0071 ELECTRICAL POWER SYSTEMS AND ELECTRICAL PROPULSION

PSCAD COURSEWORK

Author:
Hasha Dar

Module coordinator:
Prof. Richard Bucknall

November 30, 2022

Contents

List of Figures	2
List of Tables	2
1 Diode bridge circuit	3
1.1 Circuit diagram	3
1.2 Instantaneous voltages	3
1.3 Effect of increasing capacitance to 25 μF	4
2 Equivalent transformer	5
2.1 Circuit diagram	5
2.2 Resistive load	5
2.2.1 RMS Voltage	5
2.2.2 Power factor	6
2.3 Inductive load	6
2.3.1 RMS Voltage	6
2.3.2 Power factor	7
2.4 Capacitive load	7
2.4.1 RMS Voltage	7
2.4.2 Power factor	7
3 Faulted 3-phase network (1)	8
3.1 Circuit diagram	8
3.2 Voltage and current waveforms	9
3.3 Discussion	9
4 Faulted 3-phase network (2)	9
4.1 Type of fault	9
4.2 Breaker circuit	10
A MATLAB code	11
A.1 Question 1	11
A.2 Question 2	11
A.3 Question 3	12

List of Figures

1	Circuit diagram to show diode bridge circuit.	3
2	Graph to show instantaneous input voltage across the voltage source.	3
3	Graph to show instantaneous output voltage across the resistive load.	4
4	Graph to show comparison between instantaneous output voltage across the resistive load for different capacitance values.	4
5	Circuit diagram to show equivalent transformer.	5
6	Voltage across load over time and value of $V_{RMS,r}$ for the time period.	5
7	Power factor over time (resistor).	6
8	Voltage across load over time and value of $V_{RMS,i}$ for the time period.	6
9	Power factor over time (inductor).	7
10	Voltage across load over time and value of $V_{RMS,c}$ for the time period.	7
11	Power factor over time (capacitor).	8
12	Circuit diagram to show distribution network.	8
13	Faulted phase voltages over time from 0.4 s to 0.65 s.	9
14	Faulted phase currents over time from 0.4 s to 0.65 s.	9
15	Circuit diagram to show distribution network with circuit breaker.	10
16	Sequencer diagram to show breaker activation logic.	10

List of Tables

1 Diode bridge circuit

1.1 Circuit diagram

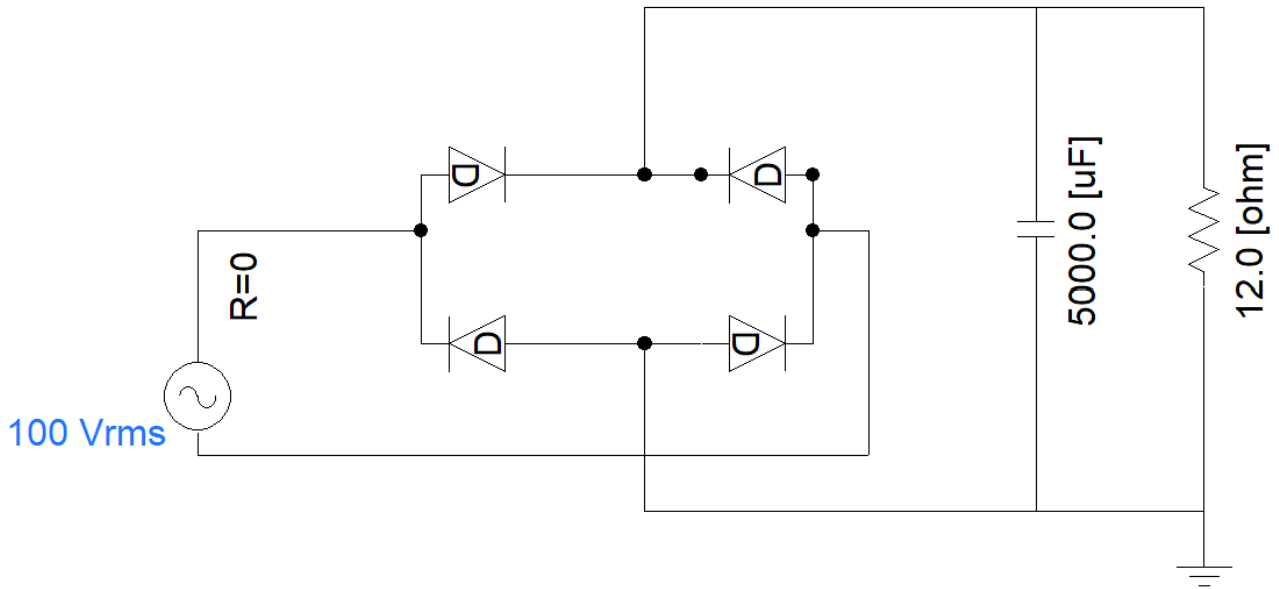


Figure 1: Circuit diagram to show diode bridge circuit.

1.2 Instantaneous voltages

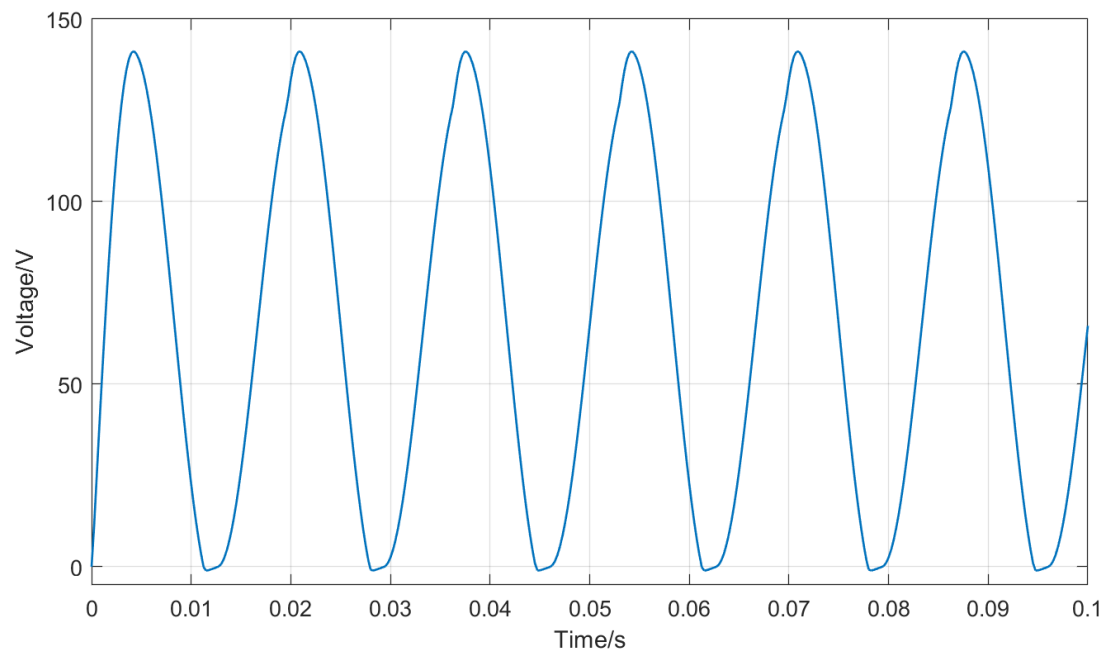


Figure 2: Graph to show instantaneous input voltage across the voltage source.

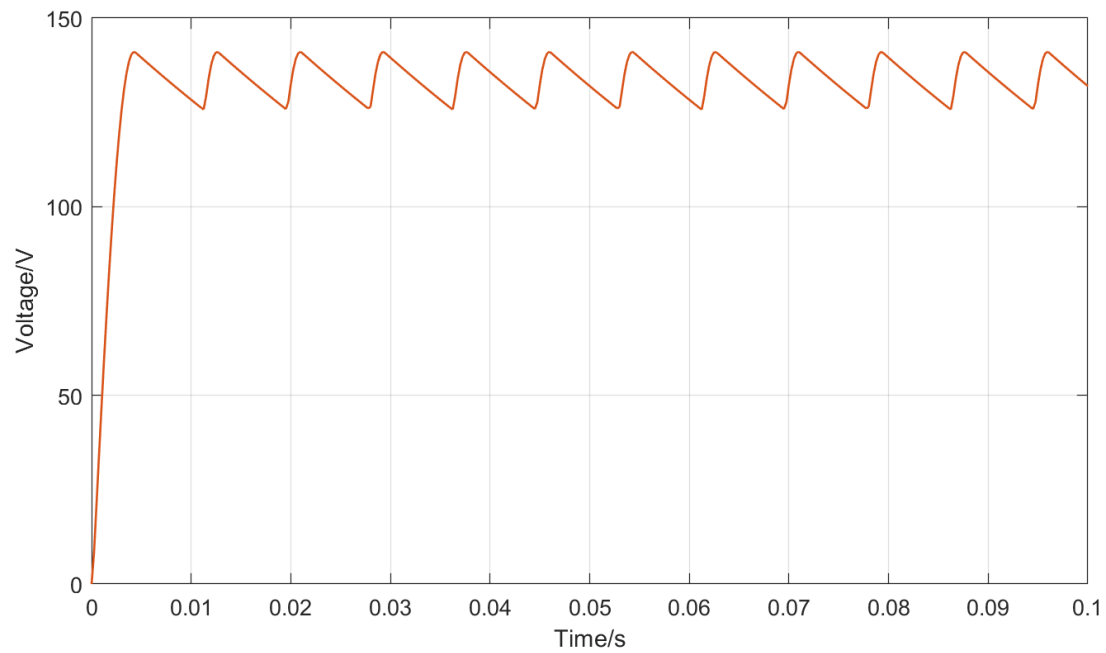


Figure 3: Graph to show instantaneous output voltage across the resistive load.

1.3 Effect of increasing capacitance to 25 μF

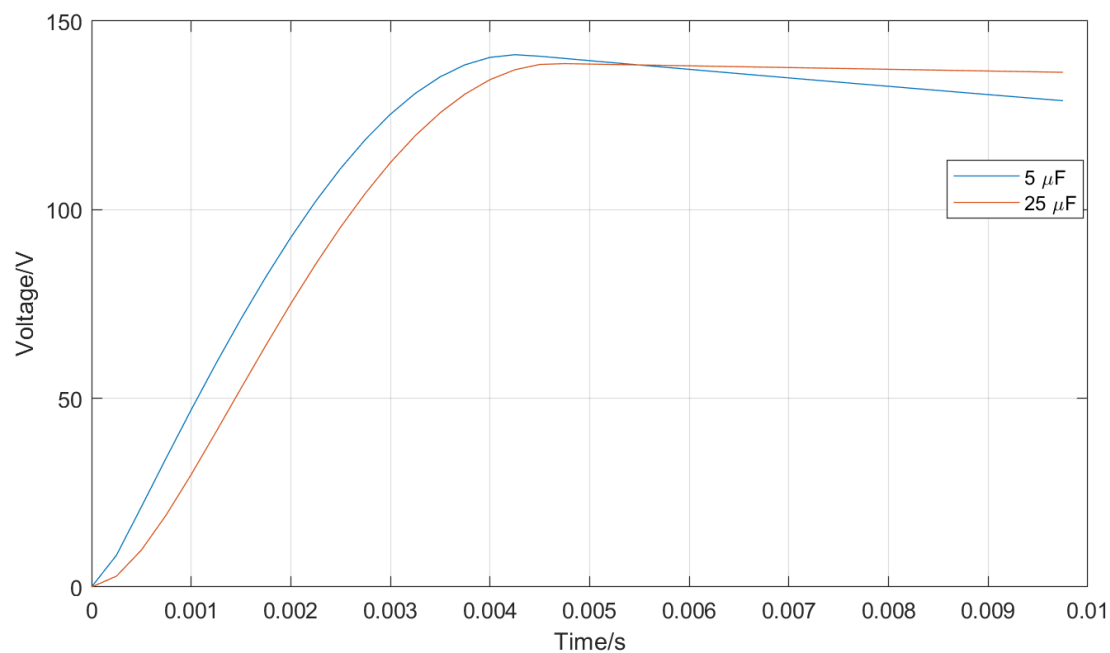


Figure 4: Graph to show comparison between instantaneous output voltage across the resistive load for different capacitance values.

The purpose of the capacitor in this diode bridge circuit is to filter/reduce the amount of voltage ripple, inherent to bridge diode circuits. We can see in Figure 3 that our voltage drop is approximately 25 V between pulses (5 μF). By increasing the capacitance, our voltage drop reduces (from data: voltage drop with 25 μF \approx 4 V.) This is desirable as this achieves a more stable DC output. However, increasing the capacitance also increases the rise time and reduces the peak voltage of the output, shown in Figure 4.

2 Equivalent transformer

2.1 Circuit diagram

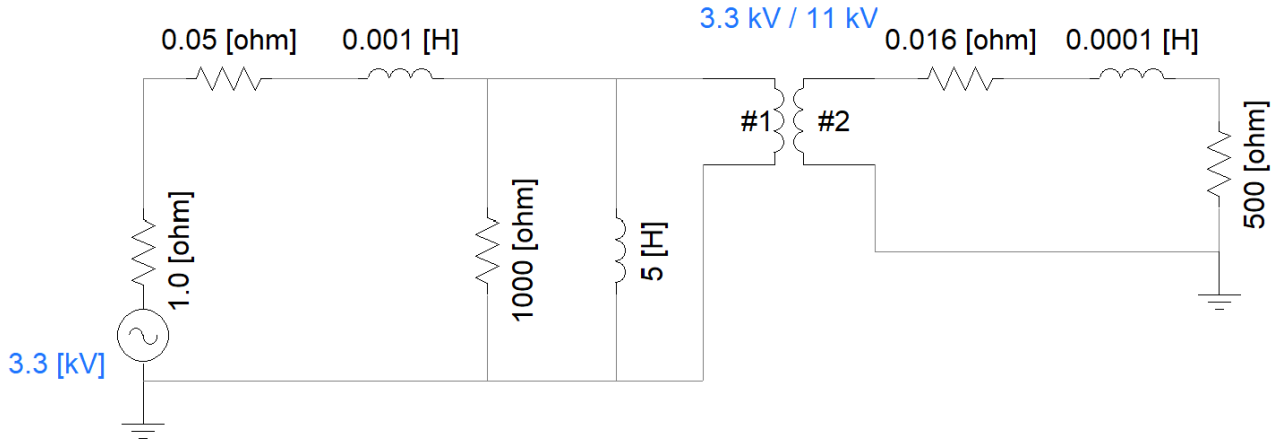


Figure 5: Circuit diagram to show equivalent transformer.

2.2 Resistive load

MATLAB code for this section of the assignment can be viewed in Appendix A.2.

2.2.1 RMS Voltage

The RMS voltage can be calculated using (1).

$$V_{RMS} = \sqrt{\frac{\sum_{i=1}^n x_i^2}{n}} \quad (1)$$

- Simulation time: 0.5 s
- Number of data points (n): 2002

Using MATLAB, the RMS voltage over the time period is:

$$V_{RMS,r} = 10.14 \text{ kV} \quad (2)$$

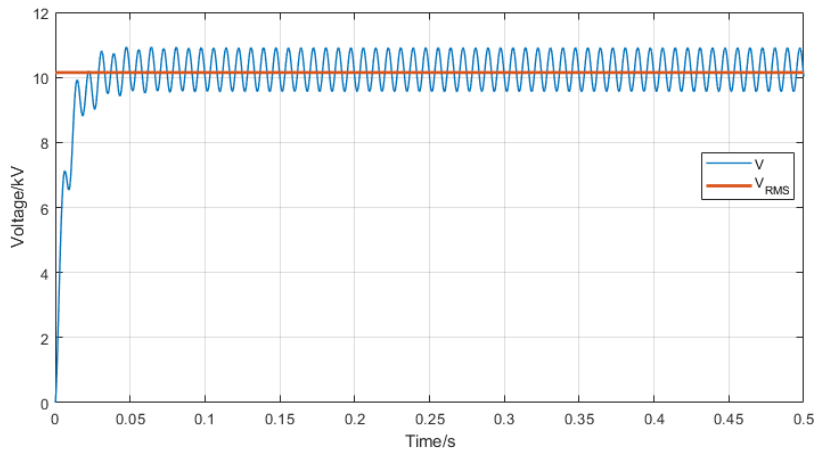


Figure 6: Voltage across load over time and value of $V_{RMS,r}$ for the time period.

2.2.2 Power factor

The power factor can be calculated using the following equation:

$$PF = \cos \phi \quad (3)$$

Using MATLAB, the converged value of the power factor was found by averaging the final values in the dataset.

$$PF_r = 0.995 \quad (4)$$

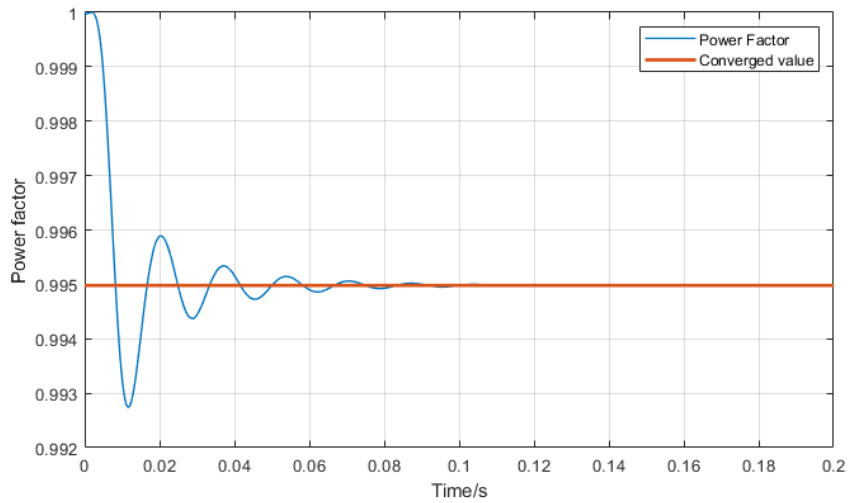


Figure 7: Power factor over time (resistor).

2.3 Inductive load

2.3.1 RMS Voltage

Using MATLAB, the RMS voltage over the time period is:

$$V_{RMS,i} = 2.79 \text{ kV} \quad (5)$$

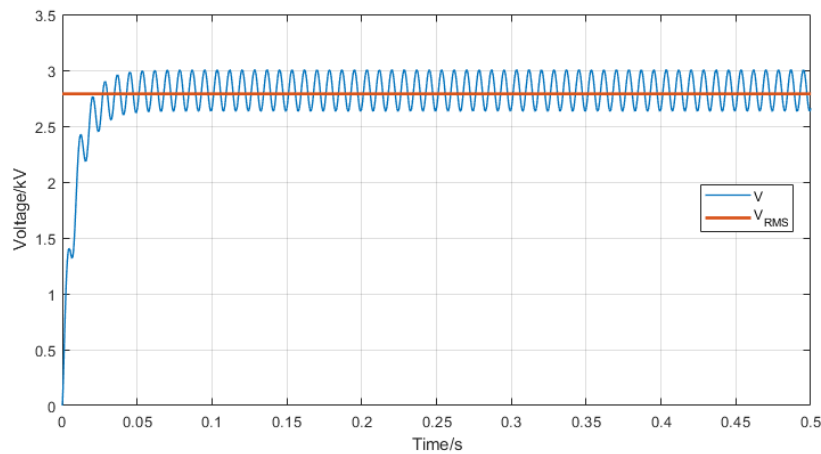


Figure 8: Voltage across load over time and value of $V_{RMS,i}$ for the time period.

2.3.2 Power factor

Using MATLAB:

$$PF_i = 0.563 \quad (6)$$

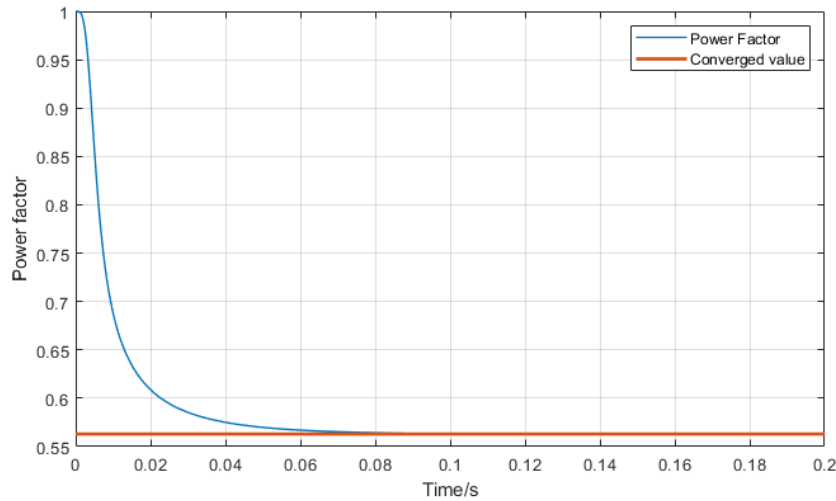


Figure 9: Power factor over time (inductor).

2.4 Capacitive load

2.4.1 RMS Voltage

Using MATLAB, the RMS voltage over the time period is:

$$V_{RMS,c} = 0.262 \text{ kV} \quad (7)$$

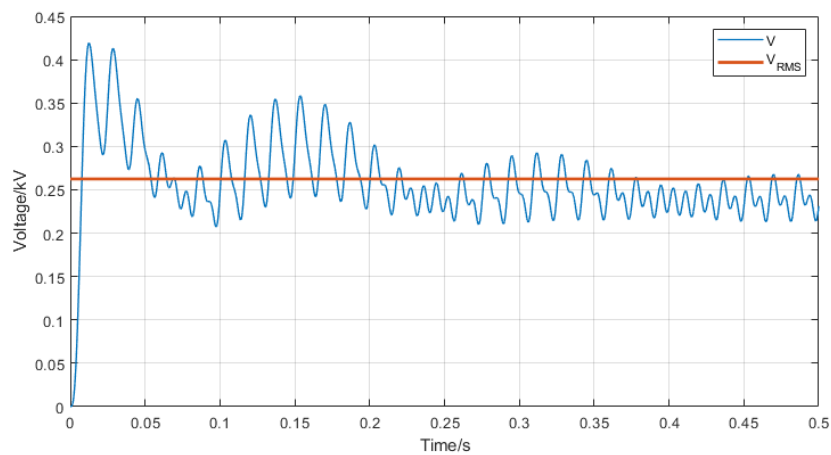


Figure 10: Voltage across load over time and value of $V_{RMS,c}$ for the time period.

2.4.2 Power factor

Using MATLAB:

$$PF_c = -0.328 \quad (8)$$

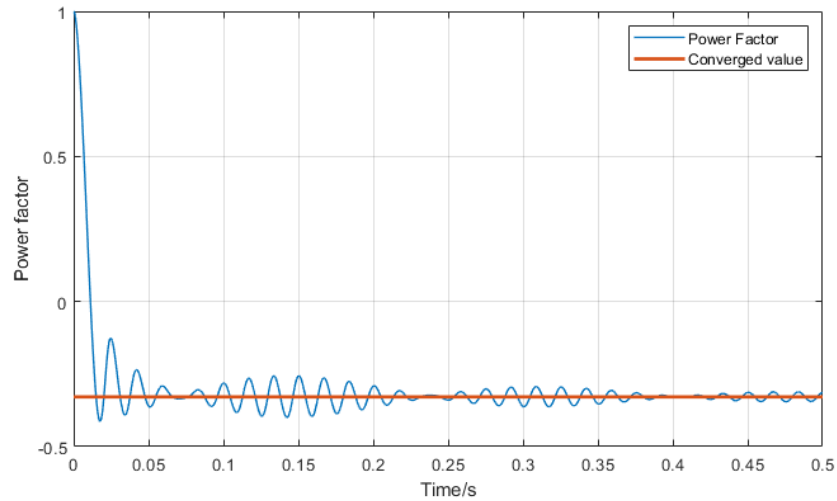


Figure 11: Power factor over time (capacitor).

3 Faulted 3-phase network (1)

3.1 Circuit diagram

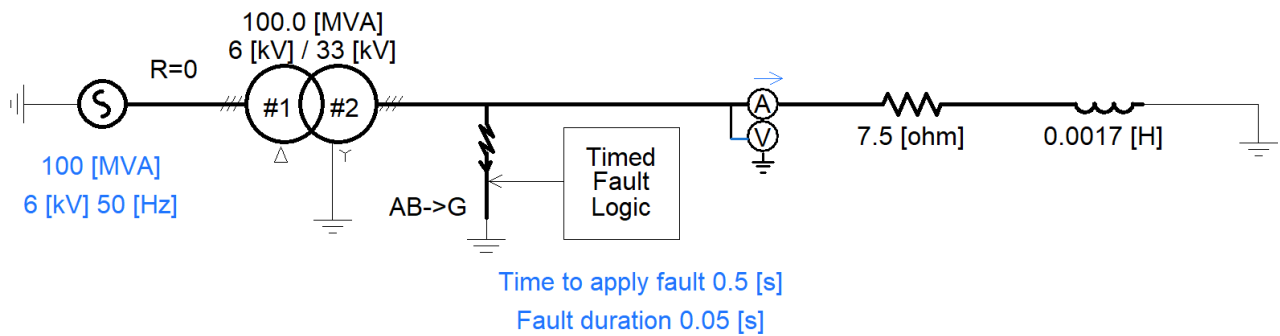


Figure 12: Circuit diagram to show distribution network.

3.2 Voltage and current waveforms

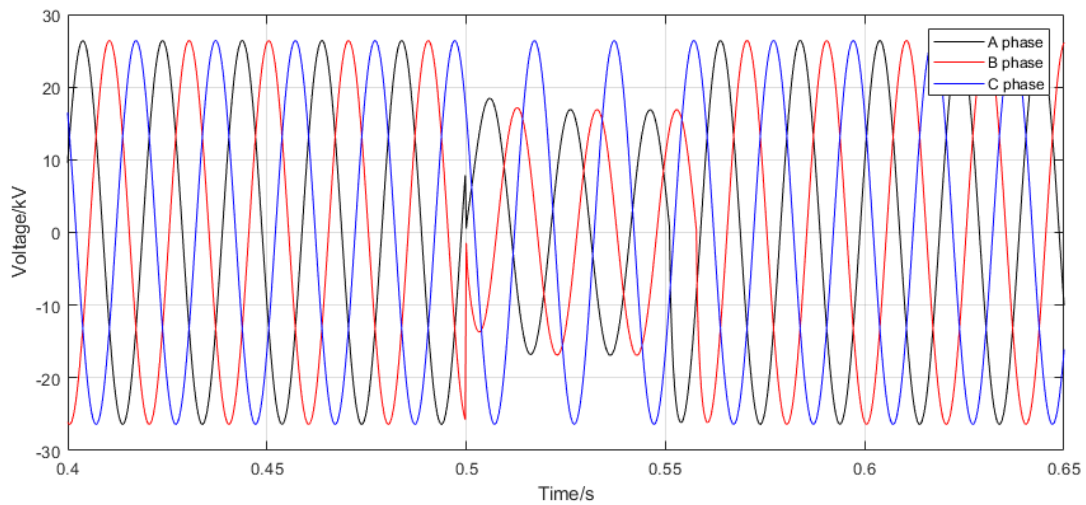


Figure 13: Faulted phase voltages over time from 0.4 s to 0.65 s.

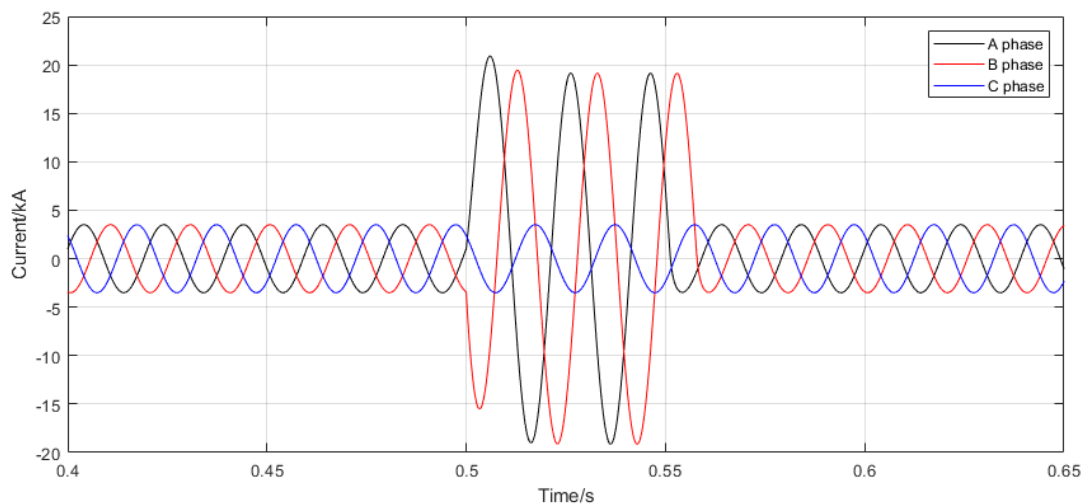


Figure 14: Faulted phase currents over time from 0.4 s to 0.65 s.

3.3 Discussion

From Figure 13, a collapse in the voltages of the faulted phases (A and B) is observed. There is no significant effect on the voltage of phase C. Phase angle is disrupted; phase A and C are 180° out of phase with respect to one another during the fault, whilst phase B is 120° out of phase with respect to phase A.

From Figure 14, the faulted phases see a considerable increase in current magnitude due to the sudden increase in ground current flow. However, all phases remain at 120° phase angle with respect to the other phases. Unfaulted phase remains unaffected.

4 Faulted 3-phase network (2)

4.1 Type of fault

From the waveforms presented in the assignment sheet, we see that as the fault occurs, the phase A and B voltages collapse, whilst the phase C voltage remains unaffected. The phase angle of A and B becomes the

same and is 180° out of phase with respect to C. In terms of the current, we see that there is a significant increase in current magnitude in phase A and B. They are also 180° out of phase with each other. The unfaulted phase remains as is. We also see that there is no significant ground current in the faulted phases.

In terms of the standard fault sequence connections, the above can be summarised as:

$$V_a = V_b \quad (9)$$

$$\therefore V_1 = V_2 \quad (10)$$

$$I_a = -I_b \quad (11)$$

$$I_c \ll I_a \quad (12)$$

$$I_0 = 0 \quad (13)$$

$$\therefore I_c = I_1 + I_2 \quad (14)$$

where subscript a, b, c represents phase and subscript 1, 2, 0 represents positive, negative and zero sequence. Hence, the analysis is indicative of a line-to-line fault, occurring on phases A and B.

4.2 Breaker circuit

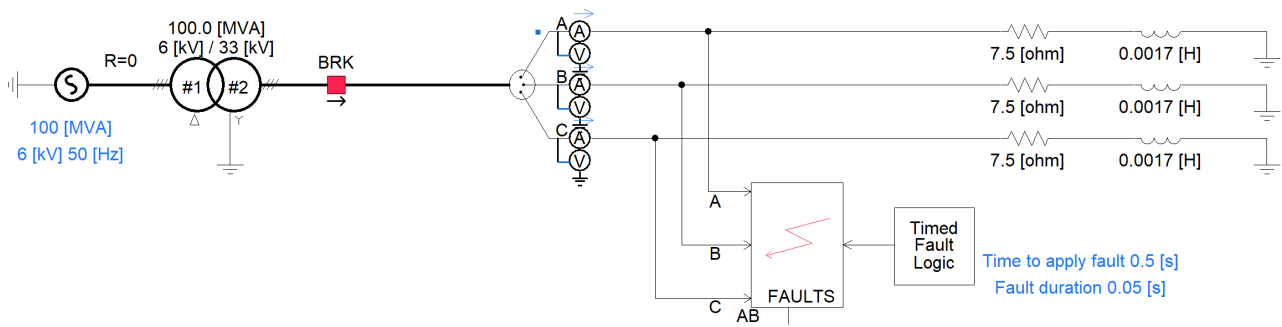


Figure 15: Circuit diagram to show distribution network with circuit breaker.

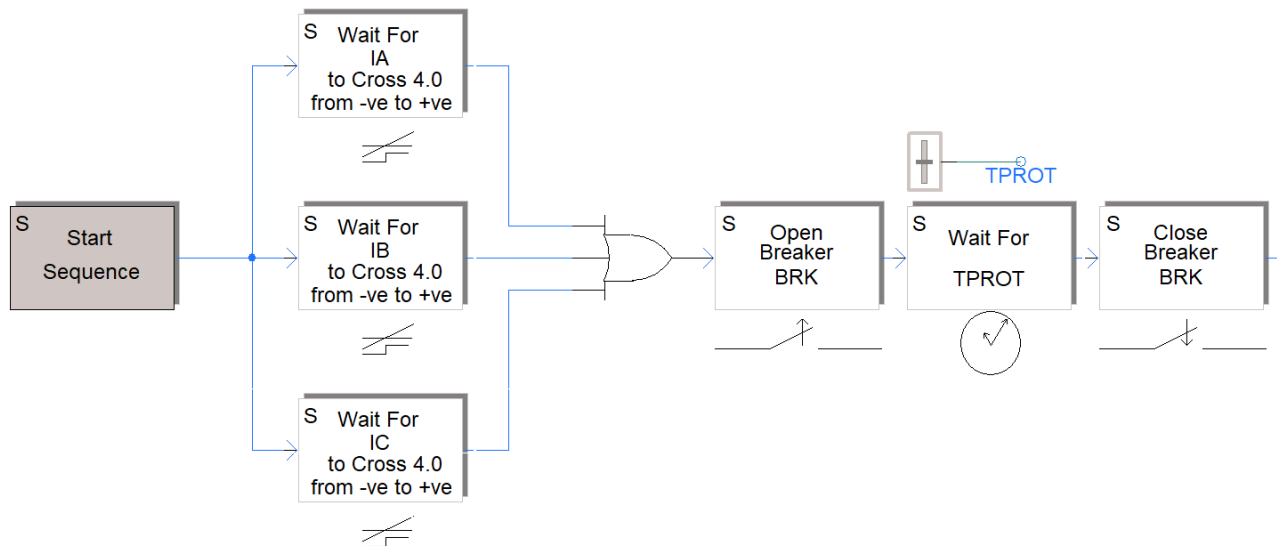


Figure 16: Sequencer diagram to show breaker activation logic.

A MATLAB code

A.1 Question 1

```
%HD
clc
clear

%import data
data = readmatrix('dataimport.xlsx','Sheet','q1');

%datasets
VSource = cat(2,data(:,5),data(:,6));
VResistor = cat(2,data(:,7),data(:,8));
VResistor2 = cat(2,data(:,9),data(:,10));

%graph plots
%plot(VResistor2(:,1),VResistor2(:,2),'LineWidth',1,'color',[0.4940 0.1840
    0.5560])
plot(VResistor(1:40,1),VResistor(1:40,2),VResistor2(1:40,1),VResistor2(1:40,2))
grid on
axis 'auto xy'
xlim([0,0.01])
ylim([0,150])
xlabel('Time/s')
ylabel('Voltage/V')
legend('5 {\mu}F','25 {\mu}F')

%'color',[0.4940 0.1840 0.5560]
```

A.2 Question 2

```
%HD
clc
clear

%import data
data = readmatrix('dataImport.xlsx','Sheet','table2');
data2 = readmatrix('dataImport.xlsx','Sheet','table2.2');

%datasets
VResistor = cat(2,data(:,1),data(:,2));
PhaseResistor = cat(2,data(:,3),data(:,4));
VInductor = cat(2,data2(:,1),data2(:,2));
PhaseInductor = cat(2,data2(:,3),data2(:,4));
VCapacitor = cat(2,data2(:,5),data2(:,6));
PhaseCapacitor = cat(2,data2(:,7),data2(:,8));

%VRMS
VSq1 = VResistor(:,2).^2;
VRMSResistor = sqrt(sum(VSq1)/numel(VSq1));

VSq2 = VInductor(:,2).^2;
VRMSInductor = sqrt(sum(VSq2)/numel(VSq2));

VSq3 = VCapacitor(:,2).^2;
VRMSCapacitor = sqrt(sum(VSq3)/numel(VSq3));

%PF
```

```
averagePFResistor =  
    cos(mean(PhaseResistor(0.8*numel(PhaseResistor(:,1)):end,2)));  
PFResistor = cos(PhaseResistor(:,2));  
  
averagePFInductor =  
    cos(mean(PhaseInductor(0.8*numel(PhaseInductor(:,1)):end,2)));  
PFInductor = cos(PhaseInductor(:,2));  
  
averagePFCapacitor =  
    cos(mean(PhaseCapacitor(0.8*numel(PhaseCapacitor(:,1)):end,2)));  
PFCapacitor = cos(PhaseCapacitor(:,2));  
  
%graph plotting  
%{  
plot(VCapacitor(:,1),VCapacitor(:,2),...  
    VCapacitor(:,1),linspace(VRMSCapacitor,VRMSCapacitor,numel(VCapacitor(:,1))))  
grid on  
axis 'auto xy'  
xlim([0,0.5])  
xlabel('Time/s')  
ylabel('Voltage/kV')  
legend('V','V_{RMS}')
```

```
%}  
  
plot(PhaseResistor(:,1),PFResistor,PhaseResistor(:,1),...  
    linspace(averagePFResistor,averagePFResistor,numel(PhaseResistor(:,1))))  
grid on  
axis 'auto xy'  
xlim([0,0.2])  
xlabel('Time/s')  
ylabel('Power factor')  
legend('Power Factor','Converged value')
```

A.3 Question 3

```
%HD  
clc  
clear  
  
%import data  
data = readmatrix('data4');  
  
%split data  
%line voltages  
V_A = cat(2,data(:,1),data(:,2));  
V_B = cat(2,data(:,1),data(:,4));  
V_C = cat(2,data(:,1),data(:,6));  
  
%line currents  
I_A = cat(2,data(:,1),data(:,3));  
I_B = cat(2,data(:,1),data(:,5));  
I_C = cat(2,data(:,1),data(:,7));  
  
%graph plotting  
  
plot(V_A(:,1),V_A(:,2),'black',...  
    V_B(:,1),V_B(:,2),'red',...  
    V_C(:,1),V_C(:,2),'blue')  
xlim([0.4,0.65])
```

```
grid on
xlabel('Time/s')
ylabel('Voltage/kV')
legend('A phase','B phase','C phase')

%{
plot(I_A(:,1),I_A(:,2),'black',...
      I_B(:,1),I_B(:,2),'red',...
      I_C(:,1),I_C(:,2),'blue')
xlim([0.4,0.65])
grid on
xlabel('Time/s')
ylabel('Current/kA')
legend('A phase','B phase','C phase')
%}
```
